

AUDIO ELECTRONICS TEST 1

dBs

- $\text{dB} = 20\log(V_{\text{measured}}/V_{\text{ref}})$
- $\text{dBV} = 20\log(V_{\text{measured}}/1V_{\text{rms}})$
- $\text{dBu} = 20\log(V_{\text{measured}}/.775V_{\text{rms}})$

Nominal Levels

- Pro audio = +4dBu = $1.23 V_{\text{rms}}$
- Consumer = -10dBV = $.318V_{\text{rms}}$ (line level)

Dynamic Range: Difference between Noise floor and Max output level (MOL)

Signal to Noise ratio: Difference between nominal level and noise floor

Headroom: difference between nominal level and MOL

Unbalanced signal

- Two wires: hot, carrying signal, and ground
- Advantages:
 - Inexpensive
- Disadvantages:
 - Susceptible to noise
- Shielded unbalanced cable
 - Wire mesh tube which encases hot signal, blocking/reducing high frequency interference (guitar cables)
 - Still susceptible to noise, longer cable = more noise

Balanced signals

- Three wire interface: Hot, ground, and cold
 - Hot and Cold 180° out of phase
 - Noise in phase for both signals
 - Subtraction of the two signals results in effectively cancelling noise while simultaneously adding the two signals resulting in twice as large an amplitude, $(A - (-A)) = 2A$
 - Two popular methods of creating subtraction
 - Op-amps
 - Transformers
- XLRs are most common example of balanced cables.

Dealing with complex numbers

Magnitude $|R| = \sqrt{A^2 + B^2}$

Magnitude squared = $|R|^2 = A^2 + B^2$

Angle/Argument = $\tan^{-1}(B/A)$

Basic electronic components and impedance

- Resistors(R), Capacitors(C), and Inductors (L) all oppose the flow of current, this opposition is called impedance (Z)

Resistor

- Resist (-) or oppose the flow of current, absorbing energy from the source by dissipating it as heat
- Resistance of a material is a measurement of its opposition capability in ohms (Ω)
- Oppose AC currents in the same way, regardless of frequency of oscillation
- Most important things about resistors:
 - AC voltage across and current through the resistor are
 - Related linearly by Ohm's Law
 - In phase with each other
- Ohm's law works for all DC and AC voltages and currents:
 - $V = IR$
- Know series and parallel resistor formulas
- Resistor Voltage Divider
 - $V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$


Inductors

- A coil of wire that obeys Faraday's Law: current through a coil of wire creates a magnetic field that opposes the current
- Measured in Henrys (H)
- Voltage leads current by 90° phase difference
- L: inductance
- Imaginary number J
 - $J = \sqrt{-1}$
 - $J^2 = -1$
 - $1/J = -J$
- $Z_L = j \omega L$
 - $\omega = 2\pi f$
- At DC = short circuit
- At F=infinity -> open circuit

Capacitors

- Two metal plates separated by a distance, dielectric material in between
- Uses an electric field (not magnetic) to exchange energy with the source
- Measured in Farads (F)
- Current leads voltage by 90° phase difference
- C = capacitance

2nd Order High-pass Design

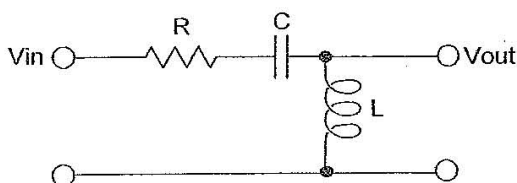


2nd Order HPF Transfer Function:

Design Equations:

Specifications: f_c, Q

- choose L
- calculate $C = \frac{1}{2\pi f_c L}$

2nd Order Low-pass Design

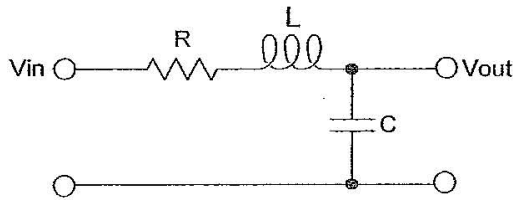

2nd Order LPF Transfer Function:

$$H(s) = \frac{1}{(s/\omega_c)^2 + (1/Q)(s/\omega_c) + 1}$$

where

$$\omega_c = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Design Equations:

Specifications: f_c, Q

1. choose L

2. calculate $C = \frac{\left(\frac{1}{2\pi f_c}\right)^2}{L}$


3. calculate $R = \frac{1}{Q} \sqrt{\frac{L}{C}}$

Special Names for Q Values

Q	Name
0.577	Bessel
0.707	Butterworth
> 0.707	Chebyshev
< 0.707	Over-damped
> 0.707	Under-damped

First Order

V_{IN}

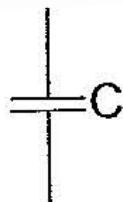

Transfer Function = $H(j\omega) = \frac{1}{1 + j\omega RC}$

$$|H(\omega)|^2 = \left(\frac{1}{1 + j\omega RC} \right) \left(\frac{1}{1 - j\omega RC} \right)$$

$$|H(\omega)|^2 = \frac{1}{1 + (\omega RC)^2}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$


1st Order LPF Transfer Function

$$H(s) = \frac{1}{1 + s/\omega_c}$$

where

$$\omega_c = \frac{1}{RC}$$

First Order High-pass Filter (HPF)

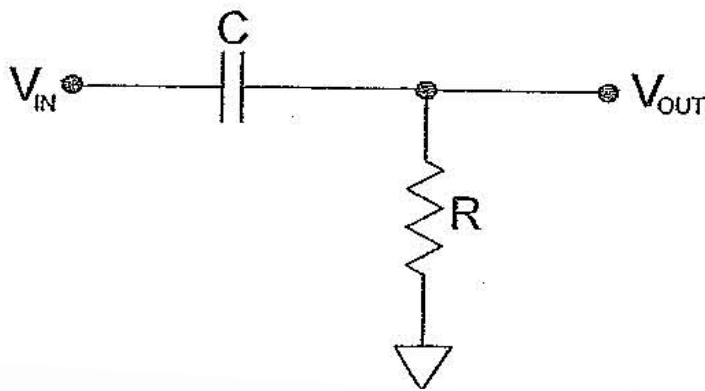

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{1}{\omega RC} \right)^2}}$$


$$f_c = \frac{1}{2\pi RC}$$

1st Order HPF Transfer Function

$$H(s) = \frac{s/\omega_c}{1 + s/\omega_c}$$

2nd Order RLC Band-pass Filter


$$\omega_c = \frac{1}{RC}$$

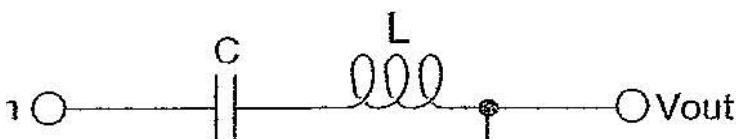

2nd Order BPF Transfer Function:

$$H(s) = \frac{(1/Q)(s/\omega_0)}{(s/\omega_0)^2 + (1/Q)(s/\omega_0) + 1}$$

2nd Order RLC Band-stop Filter

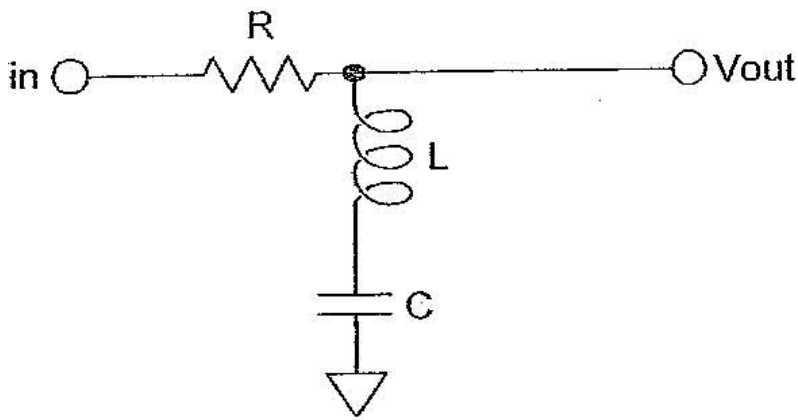

2nd Order BSF Transfer Function:

$$H(s) = \frac{(s/\omega_0)^2 + 1}{(s/\omega_0)^2 + (Q)(s/\omega_0) + 1}$$


where

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{\omega_0}{BW}$$

Shelving Filters


Low Shelving Filter

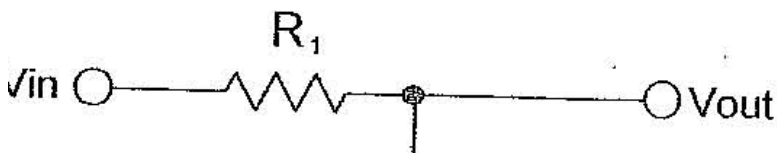

Low Shelving Transfer Function:

$$H(s) = \frac{1 + (s/\omega_b)}{1 + (s/\omega_{ir})}$$

High Shelving Filter

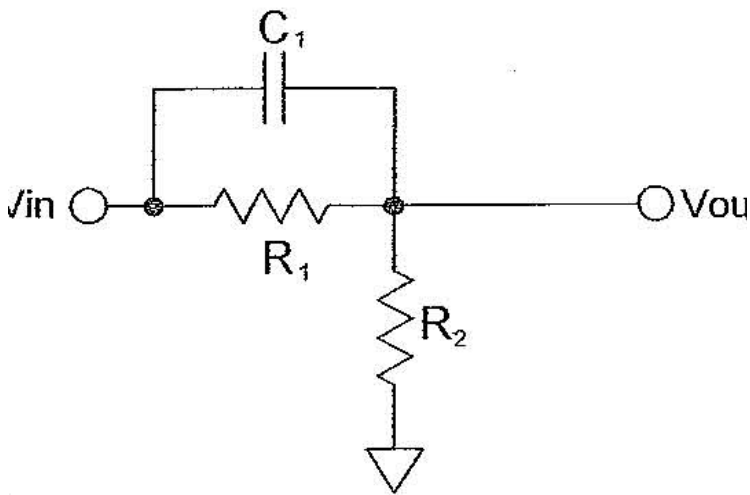

Low Shelving Transfer Function:



$$H(s) = \frac{1 + (s/\omega_L)}{1 + (s/\omega_b)}$$

$$f_b = \frac{(R_1 + R_2)}{2\pi R_1 R_2 C_1}$$


$$f_L = \frac{1}{2\pi(R_1 C_1)}$$

$$ndB = 20 \log \left(\frac{R_2}{R_1 + R_2} \right)$$


Variable Filters

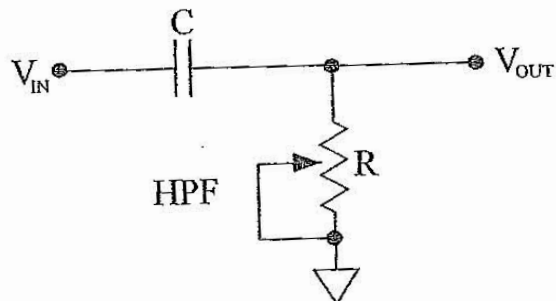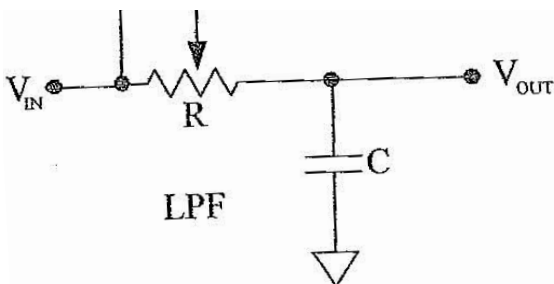


Variable Low Shelving Filter

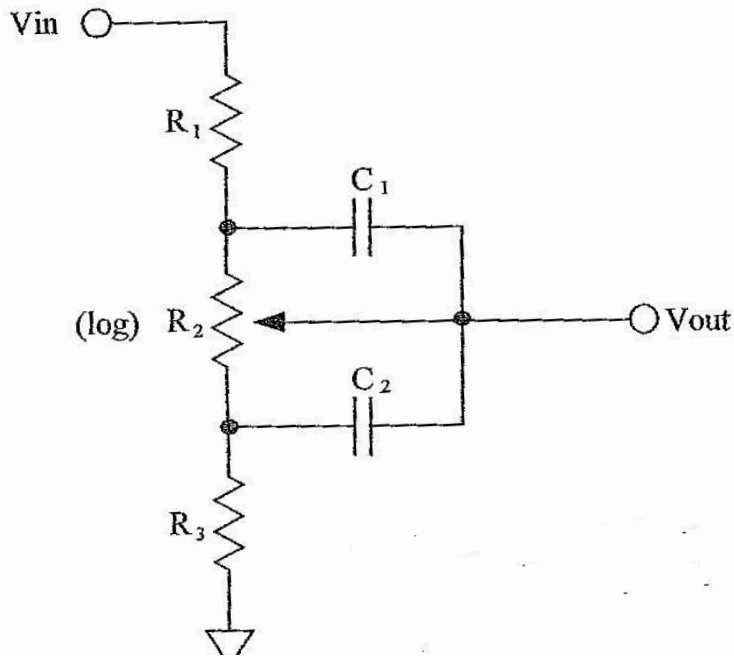


Variable High Shelving Filter

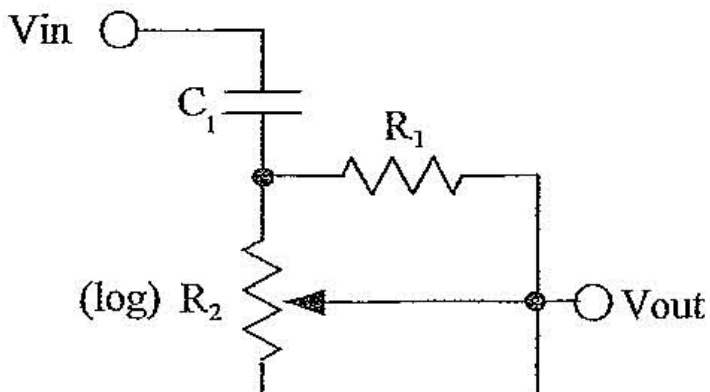


Band (Combination) Shelving Filter

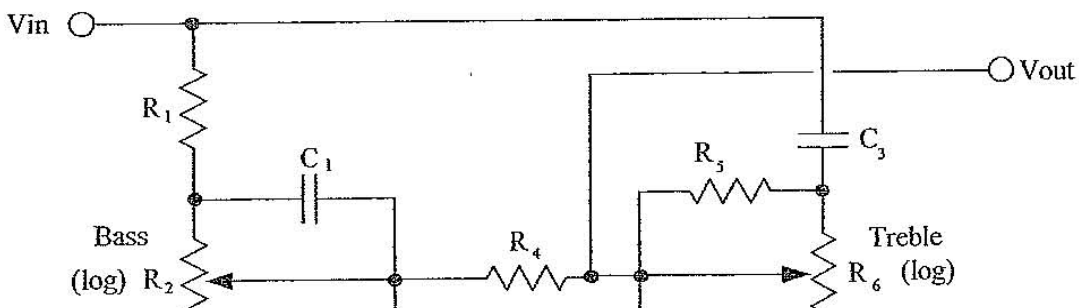

Guitar and Bass Tone Controls

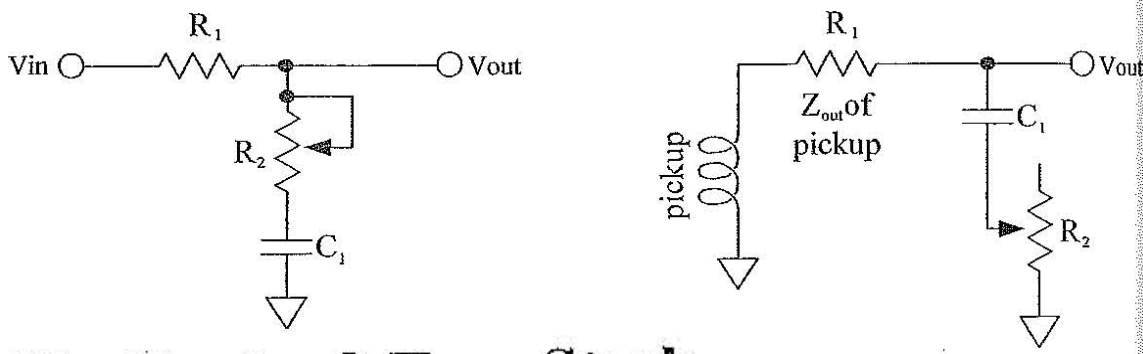



The Fender® Tone Stack

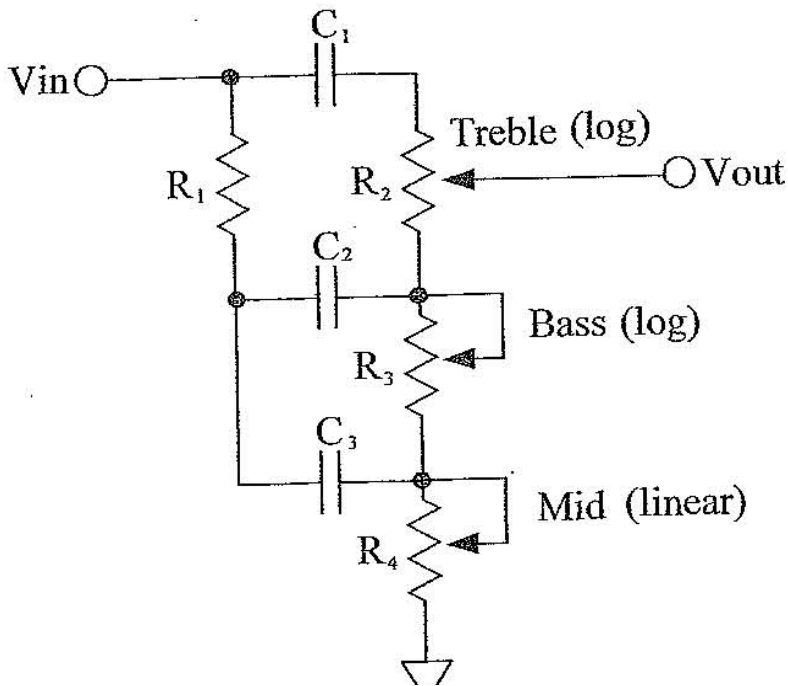

Impedance Required)



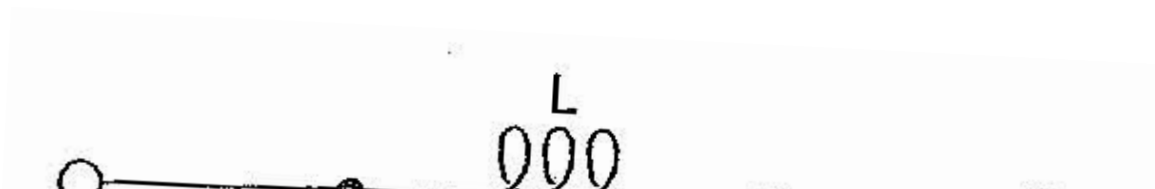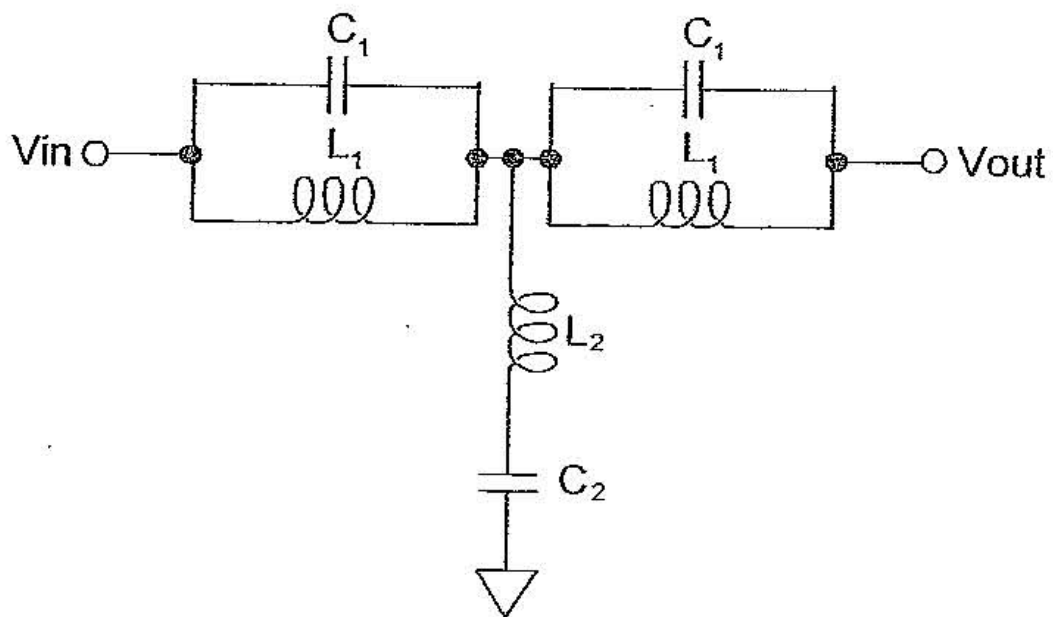6th Order BSF (Matched Line Impedance Required)



3rd Order HPF (Matched Line Impedance Required)

