



Signature Analyzer

Presented By :

**Andrew O'Neil-Smith, Amy Zamon, Austin Clifton
EEN 315 – Group 2**

**For : Sayan Maity, TA
University of Miami
November 18, 2013**



Project Goals

- Understand Shift Registers
- Reinforce sequential design
- Introduce concepts of testing, signature generation, and pseudo random binary sequence generation
- Move away from physical breadboard implementation to digital design



Background Information

- A Flip-Flop is the basic memory unit of a sequential circuit
- Types – Set/Reset, D, JK, Edge Triggered (clock) vs. Latch (signal level)
- Signatures are used to verify correct transfer of data
- Basic logic diagrams, truth table construction, Next State Tables
- Understanding of multiplexors

Background Information

- Basic understanding of truth tables, logic diagrams, transition tables, and next state tables is essential to understanding logic derivations
- Truth table for a JK flip-flop:

J	K	Q(t+1)	
0	0	Q(t)	No Change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

- Equation for a JK flip-flop: $Q^+ = JQ' + K'Q$
- Bit shifting: 0110 shifted left = 1100, 1011 shifted right = 0101, etc.

Equipment


DESCRIPTION	QUANTITY
2:1 Multiplexer	8
D Flip Flop	4
XOR Gate	2

Design Process



- Each Flip Flop represents a bit in the register, output of one is input of the next
- 2:1 MUX for each Flip Flop determines Parallel or Serial Input
- 2:1 MUX for each Flip Flop determines Right or Left Shift
- Parallel output is the output of the Flip Flops
- Signature Analyzer: XOR the two least significant bits
 $Q_{d+} = (Q_a \text{ XOR } Q_b) \text{ XOR PROBE}$
 $Q_{c+} = Q_d$
 $Q_{b+} = Q_c$
 $Q_{a+} = Q_b$
- After 10 clock cycles, will have final signature

Logic Diagram

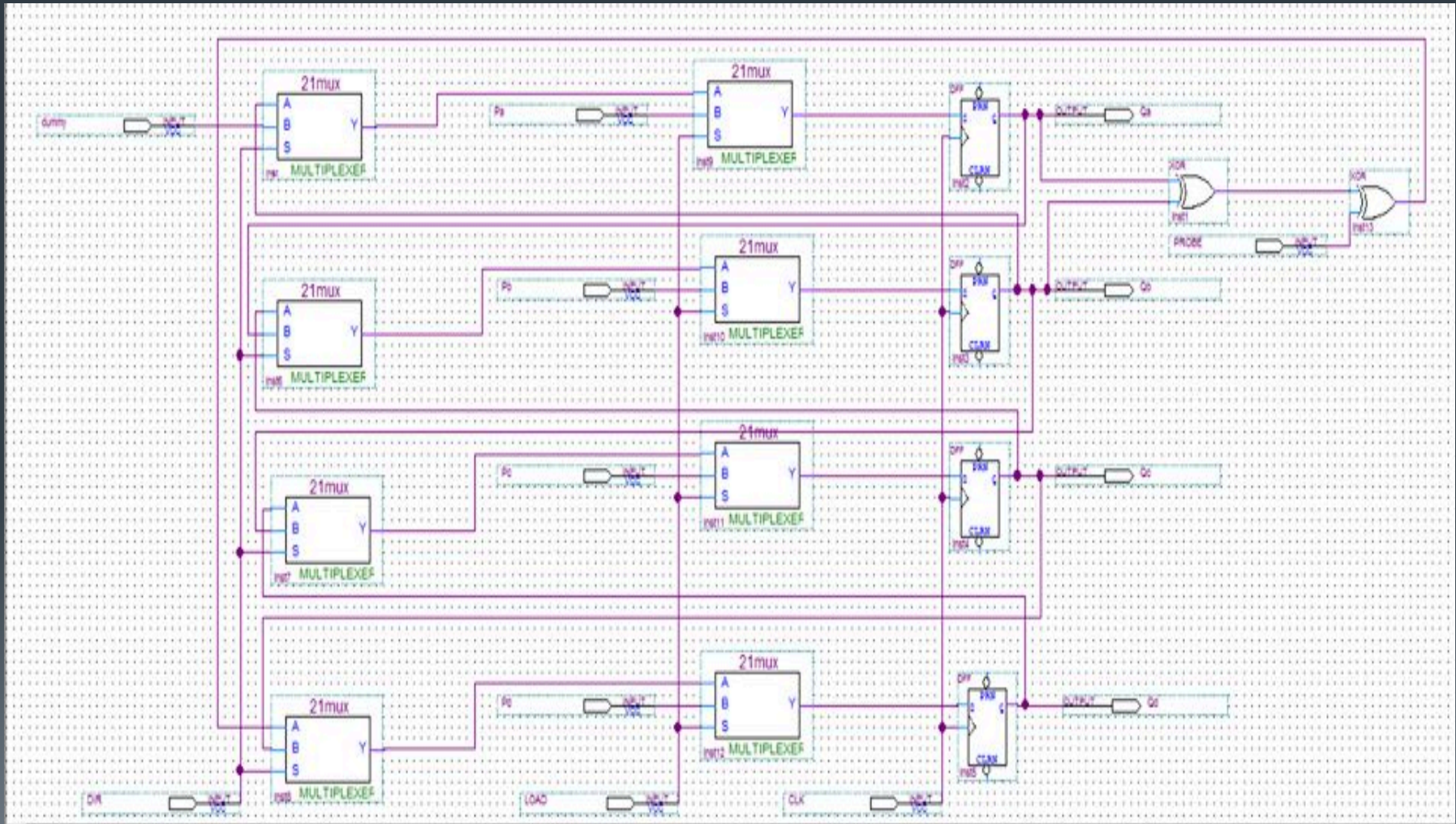



Implementation


- Design Block Diagram File
- Compilation
- Input values for Vector Waveform File
- Simulation

Sequence 1



Qd	Qc	Qb	Qa	PROBE(INPUT)	Qd+	Qc+	Qb+	Qa+
0	0	0	0	1	1	0	0	0
1	0	0	0	0	0	1	0	0
0	1	0	0	1	1	0	1	0
1	0	1	0	0	1	1	0	1
1	1	0	1	1	0	1	1	0
0	1	1	0	0	1	0	1	1
1	0	1	1	1	1	1	0	1
1	1	0	1	0	1	1	1	0
1	1	1	0	1	0	1	1	1
0	1	1	1	0	0	0	1	1

Sequence 1 Simulation

 


Sequence 2



Qd	Qc	Qb	Qa	PROBE(INPUT)	Qd+	Qc+	Qb+	Qa+
0	0	0	0	1	1	0	0	0
1	0	0	0	1	1	1	0	0
1	1	0	0	0	0	1	1	0
0	1	1	0	0	1	0	1	1
1	0	1	1	1	1	1	0	1
1	1	0	1	1	0	1	1	0
0	1	1	0	0	1	0	1	1
1	0	1	1	0	0	1	0	1
0	1	0	1	1	0	0	1	0
0	0	1	0	1	0	0	0	1

Sequence 2 Simulation

 


Sequence 3



Qd	Qc	Qb	Qa	PROBE(INPUT)	Qd+	Qc+	Qb+	Qa+
0	0	0	0	1	1	0	0	0
1	0	0	0	1	1	1	0	0
1	1	0	0	1	1	1	1	0
0	1	1	0	1	0	1	1	1
0	1	1	1	0	0	0	1	1
0	0	1	1	0	0	0	0	1
0	0	0	1	0	1	0	0	0
1	0	0	0	0	0	1	0	0
0	1	0	0	1	1	0	1	0
1	0	1	0	1	0	1	0	1

Sequence 3 Simulation

 

Sequence 4



Qd	Qc	Qb	Qa	PROBE(INPUT)	Qd+	Qc+	Qb+	Qa+
0	0	0	0	1	1	0	0	0
1	0	0	0	1	1	1	0	0
1	1	0	0	1	1	1	1	0
1	1	1	0	1	0	1	1	1
0	1	1	1	1	1	0	1	1
1	0	1	1	1	1	1	0	1
1	1	0	1	1	0	1	1	0
0	1	1	0	1	0	0	1	1
0	0	1	1	0	0	0	0	1
0	0	0	1	0	1	0	0	0

Sequence 4 Simulation





Conclusions

- Learned how to use Quartus software to design and implement circuits with simulations.
- Mistakes made initially due to lack of familiarity with Quartus software were easily found and fixed as we continued to accustom to wiring a circuit digitally, and we eventually found that wiring digitally is even easier than wiring manually on a bread board.
- Successfully implemented a shift register and shift analyzer without any major issues.